 



Term Project Report Part 1

1. Synthesis(Viterbi decoder)

a. RTL schematic



b. Post mapping schematic

 

c. Resource usage

	Resource	Usage
1	▼ Estimated ALUTs Used	355
1	-- Combinational ALUTs	355
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	239
3		
4	► Estimated ALUTs Unavailable	57
5		
6	Total combinational functions	355
7	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	8
2	-- 6 input functions	62
3	-- 5 input functions	14
4	-- 4 input functions	10
5	-- <=3 input functions	261
8		
9	▼ Combinational ALUTs by mode	
1	-- normal mode	179
2	-- extended LUT mode	8
3	-- arithmetic mode	168
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	490
12		
13	► Total registers	239
14		
15		
16	I/O pins	6
17	Total MLAB memory bits	0


2. Simulation

a. transcript

```
# yaa! in = 1, out = 1, w_ct = 249, err = 00
# yaa! in = 1, out = 1, w_ct = 250, err = 00
# yaa! in = 1, out = 1, w_ct = 251, err = 00
# yaa! in = 1, out = 1, w_ct = 252, err = 00
# yaa! in = 1, out = 1, w_ct = 253, err = 00
# yaa! in = 1, out = 1, w_ct = 254, err = 00
# yaa! in = 1, out = 1, w_ct = 255, err = 00
# corrupted_bits = 0, OUT: good = 256, bad = 0
# ** Note: $stop : C:/Users/12814/Downloads/thenewestcodewhichpasstheautograder/viterbi_tx_rx_tb.sv(91)
# Time: 1045 us Iteration: 0 Instance: /viterbi_tx_rx_tb
# Break in Module viterbi_tx_rx_tb at C:/Users/12814/Downloads/thenewestcodewhichpasstheautograder/viterbi_tx_rx_tb.sv line 91
```

It's shown in the transcript that the decoder can successfully decode the input values when there is no error injection.

b. simulation waveform

 

There is always one path whose `path_cost` is 0 at each cycle, indicating that the Add-Compare-Select (ACS) units are correctly tracking the ideal (zero-error) path through the trellis.

3.Explanations

a. explain how this encoder works

This encoder implements a convolutional encoder using a FSM with 3-bit state memory, resulting in 8 possible states.

For each input bit (`d_in`), the FSM transitions to a new state and produces a 2-bit output (`d_out_reg`), based on the current state and input.

On each rising clock edge (if `enable_i` is asserted and `rst` is inactive), it updates the state by right shifting the previous bits (`cstate[2:1]`) and inserting a new bit computed as $d_in \wedge cstate[1] \wedge cstate[0]$.

The 2-bit output `d_out` is generated according to convolutional encoding rules: the first output bit is simply the input bit ($d_out[0] = d_in$), while the second is the XOR of the input and selected state bits ($d_out[1] = d_in \wedge cstate[2] \wedge cstate[1]$).

b. explain how the decoder works

The Viterbi decoder is a digital signal processing block designed to find the most likely sequence of states in a finite-state process, making it ideal for decoding convolutionally encoded data. The architecture is built from four primary components: Branch Metric Computation (BMC) units, Add-Compare-Select (ACS) units, Trellis Memory banks, and Trace-Back Units (TBU).

The BMC units calculate the branch metric for each possible state transition in the trellis. This metric is the Hamming distance between the 2-bit symbol received from the channel (`d_in`) and the ideal symbol that the encoder would have produced for that specific transition. A smaller metric indicates a closer match, meaning the transition was more likely to have occurred.

The ACS units form the core recursive engine of the decoder. For each state in the trellis, an ACS unit performs three operations:

①Add: It adds the incoming branch metric from a BMC unit to the accumulated path metric of the preceding state to calculate a new total path cost.

②Compare: It compares the total path costs of the two paths that converge at the current state.

③Select: It chooses the path with the minimum cost as the survivor path. The decision (selection) bit indicating which path was chosen is stored for later use.

The decoder uses four banks of memory to store the selection bits generated by the ACS units at each time step. This creates a record of survivor paths through the trellis over a specific depth. The memory is managed in a circular buffer fashion, allowing new decisions to be written continuously while older decisions are read for traceback.

The TBU is responsible for the final decoding step. It reads the selection bits from the trellis memory and, starting from a state with the lowest path cost (or a fixed end-state like state 0), traces the single most likely path backward through the trellis.

Based on the decisions encountered at each step of the traceback, the TBU reconstructs the original sequence of bits that were fed into the encoder, producing the final `d_out`.

c. show the minimum branch metric=0 when no errors are present


```

        wire [1:0]    bmc4_path_1_bmc;
        wire [1:0]    bmc5_path_0_bmc;
        wire [1:0]    bmc5_path_1_bmc;
        wire [1:0]    bmc6_path_0_bmc;
        wire [1:0]    bmc6_path_1_bmc;
        wire [1:0]    bmc7_path_0_bmc;
        wire [1:0]    bmc7_path_1_bmc;
//ACS modules signals
    logic [7:0]    validity;//Store path validity for each state (updated every clock
cycle)
    logic [7:0]    selection;// Store selection signal for each state
    logic [7:0]    path_cost [8];// Store path cost for each state
    wire [7:0]    validity_nets;// Concatenated valid_o outputs from 8 ACS units
    wire [7:0]    selection_nets;// Concatenated selection outputs from 8 ACS units

//wire        ACLK_selection; // K=0,1,...7                (i.e., 8 of these)
        wire        ACS0_selection;
        wire        ACS1_selection;
        wire        ACS2_selection;
        wire        ACS3_selection;
        wire        ACS4_selection;
        wire        ACS5_selection;
        wire        ACS6_selection;
        wire        ACS7_selection;

// wire        ACLK_valid_o;        // K=0,1,...7
        wire        ACS0_valid_o;
        wire        ACS1_valid_o;
        wire        ACS2_valid_o;
        wire        ACS3_valid_o;
        wire        ACS4_valid_o;
        wire        ACS5_valid_o;
        wire        ACS6_valid_o;
        wire        ACS7_valid_o;

//wire [7:0]    ACLK_path_cost; // K=0,1,...7
        wire [7:0]    ACS0_path_cost;
        wire [7:0]    ACS1_path_cost;
        wire [7:0]    ACS2_path_cost;
        wire [7:0]    ACS3_path_cost;
        wire [7:0]    ACS4_path_cost;
        wire [7:0]    ACS5_path_cost;
        wire [7:0]    ACS6_path_cost;
        wire [7:0]    ACS7_path_cost;

```

```

//Trelis memory write operation, pipeline delay
logic [1:0]    mem_bank;
logic [1:0]    mem_bank_Q;
logic [1:0]    mem_bank_Q2;
logic         mem_bank_Q3;
logic         mem_bank_Q4;
logic         mem_bank_Q5;
logic [9:0]    wr_mem_counter;
logic [9:0]    rd_mem_counter;

// 4 memory banks -- address pointers          (there are 4 of these)
//logic [9:0]    addr_mem_K; // K=A,B,C,D
    logic [9:0]    addr_mem_A;
    logic [9:0]    addr_mem_B;
    logic [9:0]    addr_mem_C;
    logic [9:0]    addr_mem_D;
// write enables
//logic         wr_mem_K; // K=A,B,C,D
    logic         wr_mem_A;
    logic         wr_mem_B;
    logic         wr_mem_C;
    logic         wr_mem_D;
// data to memories
//logic [7:0]    d_in_mem_K;    // K=A,B,C,D
    logic [7:0]    d_in_mem_A;
    logic [7:0]    d_in_mem_B;
    logic [7:0]    d_in_mem_C;
    logic [7:0]    d_in_mem_D;
// data from memories
//wire [7:0]    d_o_mem_K;    // K=A,B,C,D
    wire [7:0]    d_o_mem_A;
    wire [7:0]    d_o_mem_B;
    wire [7:0]    d_o_mem_C;
    wire [7:0]    d_o_mem_D;

//Trace back module signals
logic         selection_tbu_0;
logic         selection_tbu_1;

logic [7:0]    d_in_0_tbu_0;
logic [7:0]    d_in_1_tbu_0;
logic [7:0]    d_in_0_tbu_1;
logic [7:0]    d_in_1_tbu_1;

wire          d_o_tbu_0;
wire          d_o_tbu_1;

logic         enable_tbu_0;

```

```

    logic          enable_tbu_1;

//Display memory operations
    wire          wr_disp_mem_0;
    wire          wr_disp_mem_1;

    wire          d_in_disp_mem_0;
    wire          d_in_disp_mem_1;

    logic [9:0]    wr_mem_counter_disp;
    logic [9:0]    rd_mem_counter_disp;

    logic [9:0]    addr_disp_mem_0;
    logic [9:0]    addr_disp_mem_1;

//Branch metric calculation modules (8 total)(Branch metric calculation)

    bmc0
    bmc0_inst(.rx_pair(d_in),.path_0_bmc(bmc0_path_0_bmc),.path_1_bmc(bmc0_path
_1_bmc));
        bmc1
    bmc1_inst(.rx_pair(d_in),.path_0_bmc(bmc1_path_0_bmc),.path_1_bmc(bmc1_path
_1_bmc));
            bmc1
    bmc2_inst(.rx_pair(d_in),.path_0_bmc(bmc2_path_0_bmc),.path_1_bmc(bmc2_path
_1_bmc));
                bmc0
    bmc3_inst(.rx_pair(d_in),.path_0_bmc(bmc3_path_0_bmc),.path_1_bmc(bmc3_path
_1_bmc));
                    bmc0
    bmc4_inst(.rx_pair(d_in),.path_0_bmc(bmc4_path_0_bmc),.path_1_bmc(bmc4_path
_1_bmc));
                        bmc1
    bmc5_inst(.rx_pair(d_in),.path_0_bmc(bmc5_path_0_bmc),.path_1_bmc(bmc5_path
_1_bmc));
                            bmc1
    bmc6_inst(.rx_pair(d_in),.path_0_bmc(bmc6_path_0_bmc),.path_1_bmc(bmc6_path
_1_bmc));
                                bmc0
    bmc7_inst(.rx_pair(d_in),.path_0_bmc(bmc7_path_0_bmc),.path_1_bmc(bmc7_path
_1_bmc));

//K=0,1,...7
/*
    bmc0  bmc0_inst(d_in,bmc0_path_0_bmc,bmc0_path_1_bmc);
        bmc0  bmc1_inst(d_in,bmc1_path_0_bmc,bmc1_path_1_bmc);
            bmc1  bmc2_inst(d_in,bmc2_path_0_bmc,bmc2_path_1_bmc);
                bmc1  bmc3_inst(d_in,bmc3_path_0_bmc,bmc3_path_1_bmc);

```

```

        bmc1  bmc4_inst(d_in,bmc4_path_0_bmc,bmc4_path_1_bmc);
        bmc1  bmc5_inst(d_in,bmc5_path_0_bmc,bmc5_path_1_bmc);
        bmc0  bmc6_inst(d_in,bmc6_path_0_bmc,bmc6_path_1_bmc);
        bmc0  bmc7_inst(d_in,bmc7_path_0_bmc,bmc7_path_1_bmc);
    */
//Add Compare Select Modules (8 copies -- note pattern in connections!!)
// i = 0, 1, ... 7      j = 0, 3, 4, 7, 1, 2, 5, 6      k = 1, 2, 5, 6, 0, 3, 4, 7 -- these create
lattice butterfly connection pattern
    //ACS
    ACSi(validity[j],validity[k],bmci_path_i_bmc,bmci_path_1_bmc,path_cost[j],path_cost[
k],ACSi_selection,ACSi_valid_o,ACSi_path_cost);
    ACS ACS0 (
        .path_0_valid(validity[0]),
        .path_1_valid(validity[1]),
        .path_0_bmc(bmc0_path_0_bmc),
        .path_1_bmc(bmc0_path_1_bmc),
        .path_0_pmc(path_cost[0]),
        .path_1_pmc(path_cost[1]),
        .selection(ACS0_selection),
        .valid_o(ACS0_valid_o),
        .path_cost(ACS0_path_cost));
        ACS ACS1 (
        .path_0_valid(validity[3]),
        .path_1_valid(validity[2]),
        .path_0_bmc(bmc1_path_0_bmc),
        .path_1_bmc(bmc1_path_1_bmc),
        .path_0_pmc(path_cost[3]),
        .path_1_pmc(path_cost[2]),
        .selection(ACS1_selection),
        .valid_o(ACS1_valid_o),
        .path_cost(ACS1_path_cost));
    ACS ACS2 (
        .path_0_valid(validity[4]),
        .path_1_valid(validity[5]),
        .path_0_bmc(bmc2_path_0_bmc),
        .path_1_bmc(bmc2_path_1_bmc),
        .path_0_pmc(path_cost[4]),
        .path_1_pmc(path_cost[5]),
        .selection(ACS2_selection),
        .valid_o(ACS2_valid_o),
        .path_cost(ACS2_path_cost));
        ACS ACS3 (
        .path_0_valid(validity[7]),
        .path_1_valid(validity[6]),
        .path_0_bmc(bmc3_path_0_bmc),
        .path_1_bmc(bmc3_path_1_bmc),
        .path_0_pmc(path_cost[7]),
        .path_1_pmc(path_cost[6]),

```



```

.selection(ACS3_selection),
.valid_o(ACS3_valid_o),
.path_cost(ACS3_path_cost));
    ACS ACS4 (
.path_0_valid(validity[1]),
.path_1_valid(validity[0]),
.path_0_bmc(bmc4_path_0_bmc),
.path_1_bmc(bmc4_path_1_bmc),
.path_0_pmc(path_cost[1]),
.path_1_pmc(path_cost[0]),
.selection(ACS4_selection),
.valid_o(ACS4_valid_o),
.path_cost(ACS4_path_cost));
    ACS ACS5 (
.path_0_valid(validity[2]),
.path_1_valid(validity[3]),
.path_0_bmc(bmc5_path_0_bmc),
.path_1_bmc(bmc5_path_1_bmc),
.path_0_pmc(path_cost[2]),
.path_1_pmc(path_cost[3]),
.selection(ACS5_selection),
.valid_o(ACS5_valid_o),
.path_cost(ACS5_path_cost));
ACS ACS6 (
.path_0_valid(validity[5]),
.path_1_valid(validity[4]),
.path_0_bmc(bmc6_path_0_bmc),
.path_1_bmc(bmc6_path_1_bmc),
.path_0_pmc(path_cost[5]),
.path_1_pmc(path_cost[4]),
.selection(ACS6_selection),
.valid_o(ACS6_valid_o),
.path_cost(ACS6_path_cost));
    ACS ACS7 (
.path_0_valid(validity[6]),
.path_1_valid(validity[7]),
.path_0_bmc(bmc7_path_0_bmc),
.path_1_bmc(bmc7_path_1_bmc),
.path_0_pmc(path_cost[6]),
.path_1_pmc(path_cost[7]),
.selection(ACS7_selection),
.valid_o(ACS7_valid_o),
.path_cost(ACS7_path_cost));
// validity_nets = // same for ACSK_valid_os
assign selection_nets = {ACS7_selection, ACS6_selection, ACS5_selection,
ACS4_selection, ACS3_selection, ACS2_selection, ACS1_selection,
ACS0_selection};

```

```

assign validity_nets = {ACS7_valid_o, ACS6_valid_o, ACS5_valid_o,
ACS4_valid_o, ACS3_valid_o, ACS2_valid_o, ACS1_valid_o, ACS0_valid_o};

```

```

always @ (posedge clk, negedge rst) begin
    if(!rst) begin
        validity      <= 8'b1;
        selection     <= 8'b0;
        // clear all 8 path costs
        path_cost[0]  <= 8'd0;
                        path_cost[1]  <= 8'd0;
                        path_cost[2]  <= 8'd0;
                        path_cost[3]  <= 8'd0;
                        path_cost[4]  <= 8'd0;
                        path_cost[5]  <= 8'd0;
                        path_cost[6]  <= 8'd0;
                        path_cost[7]  <= 8'd0;
    end
    else if(!enable) begin
        validity      <= 8'b1;
        selection     <= 8'b0;
        // clear all 8 path costs
        path_cost[0]  <= 8'd0;
                        path_cost[1]  <= 8'd0;
                        path_cost[2]  <= 8'd0;
                        path_cost[3]  <= 8'd0;
                        path_cost[4]  <= 8'd0;
                        path_cost[5]  <= 8'd0;
                        path_cost[6]  <= 8'd0;
                        path_cost[7]  <= 8'd0;
    end
    else if ( path_cost[0][7] && path_cost[1][7] && path_cost[2][7] && path_cost[3][7]
&& path_cost[4][7] && path_cost[5][7] && path_cost[6][7] && path_cost[7][7])
        begin

            validity      <= validity_nets;
            selection     <= selection_nets;
            //path_cost[K]  <= 8'b01111111 & ACSK_path_cost; // K = 0, 1, ..., 7
                        path_cost[0]  <= 8'b01111111 & ACS0_path_cost;
                        path_cost[1]  <= 8'b01111111 & ACS1_path_cost;
                        path_cost[2]  <= 8'b01111111 & ACS2_path_cost;
                        path_cost[3]  <= 8'b01111111 & ACS3_path_cost;
                        path_cost[4]  <= 8'b01111111 & ACS4_path_cost;
                        path_cost[5]  <= 8'b01111111 & ACS5_path_cost;
                        path_cost[6]  <= 8'b01111111 & ACS6_path_cost;
                        path_cost[7]  <= 8'b01111111 & ACS7_path_cost;
        end
    end
end

```

```

end
else begin
    validity    <= validity_nets;
    selection    <= selection_nets;

    //path_cost[K]    <= ACSI_path_cost;    // K = 0, 1, ..., 7
    path_cost[0]    <= ACS0_path_cost;
    path_cost[1]    <= ACS1_path_cost;
    path_cost[2]    <= ACS2_path_cost;
    path_cost[3]    <= ACS3_path_cost;
    path_cost[4]    <= ACS4_path_cost;
    path_cost[5]    <= ACS5_path_cost;
    path_cost[6]    <= ACS6_path_cost;
    path_cost[7]    <= ACS7_path_cost;

end
end

//trellis memory
always @ (posedge clk, negedge rst) begin    // wr_mem_counter  Track write
counter
// if rst (active low) or not enabling (active high), force to 0; else, increment by 1
    if(!rst) wr_mem_counter <= 10'd0;
        else if(!enable) wr_mem_counter <= 10'd0;
        else wr_mem_counter <= wr_mem_counter + 1;
end

always @ (posedge clk, negedge rst) begin//Track read counter (trace back)
    if(!rst)
        rd_mem_counter <= 10'd1023;// set to max value
    else if(enable)
        rd_mem_counter <= rd_mem_counter - 1;// count down by 1
end

always @ (posedge clk, negedge rst)//When one bank is full at 1023, move to next
bank
    if(!rst)
        mem_bank <= 2'b0;
    else begin
        /*if(wr_mem_counter = -1  fill in the guts*/
            if(wr_mem_counter == 10'd1023)
                mem_bank <= mem_bank + 2'b1;
    end

always @ (posedge clk)  begin
    d_in_mem_A <= selection;    // k = A, B, C, D - all banks write the
same selection data
        d_in_mem_B <= selection;
        d_in_mem_C <= selection;

```

```

        d_in_mem_D <= selection;
    end

    // memory bank management: always write to one, read from two others, keep
    address at 0 (no writing) for fourth one
    always @ (posedge clk)    // in each case, the memory bank w/ the
    wr_mem_counter needs a write enable; all others = 0 e.g. 0-1023: Write to Bank A,
    traceback read from Bank B&D 1024-2047: Write to Bank B, traceback read from
    Bank A&C 2048-3071: Write to Bank C, traceback read from Bank B&D 3072-4095:
    Write to Bank D, traceback read from Bank A&C
    begin
        case(mem_bank)
            2'b00: begin                // write to A, clear C, read from others
                wr_mem_A <= 1'b1;
                wr_mem_B <= 1'b0;
                wr_mem_C <= 1'b0;
                wr_mem_D <= 1'b0;
                addr_mem_A <= wr_mem_counter;
                addr_mem_B <= rd_mem_counter;
                addr_mem_C <= 10'd0;
                addr_mem_D <= rd_mem_counter;
            end
            2'b01: begin                // write to B, clear D, read from others
                wr_mem_A <= 1'b0;
                wr_mem_B <= 1'b1;
                wr_mem_C <= 1'b0;
                wr_mem_D <= 1'b0;
                addr_mem_A <= rd_mem_counter;
                addr_mem_B <= wr_mem_counter;
                addr_mem_C <= rd_mem_counter;
                addr_mem_D <= 10'd0;
            end
            2'b10: begin                // write to C, clear A, read from others
                wr_mem_A <= 1'b0;
                wr_mem_B <= 1'b0;
                wr_mem_C <= 1'b1;
                wr_mem_D <= 1'b0;
                addr_mem_A <= 10'd0;
                addr_mem_B <= rd_mem_counter;
                addr_mem_C <= wr_mem_counter;
                addr_mem_D <= rd_mem_counter;
            end
            2'b11: begin                // write to D, clear B, read from others
                wr_mem_A <= 1'b0;
                wr_mem_B <= 1'b0;
                wr_mem_C <= 1'b0;
                wr_mem_D <= 1'b1;
                addr_mem_A <= rd_mem_counter;

```

```

        addr_mem_B <= 10'd0;
        addr_mem_C <= rd_mem_counter;
        addr_mem_D <= wr_mem_counter;
    end
endcase
end

```

//Trelis memory module instantiation

```

mem  trelis_mem_A      (
    .clk,
    .wr (wr_mem_A),
    .addr(addr_mem_A),
    .d_i (d_in_mem_A),
    .d_o (d_o_mem_A)
);

```

/* likewise for trelis_memB, C, D
*/

```

mem  trelis_mem_B      (
    .clk(clk),
    .wr (wr_mem_B),
    .addr(addr_mem_B),
    .d_i (d_in_mem_B),
    .d_o (d_o_mem_B)
);

```

```

mem  trelis_mem_C      (
    .clk(clk),
    .wr (wr_mem_C),
    .addr(addr_mem_C),
    .d_i (d_in_mem_C),
    .d_o (d_o_mem_C)
);

```

```

mem  trelis_mem_D      (
    .clk(clk),
    .wr (wr_mem_D),
    .addr(addr_mem_D),
    .d_i (d_in_mem_D),
    .d_o (d_o_mem_D)
);

```

//Trace back module operation

```

always @(posedge clk)
/* create mem_bank, mem_bank_Q1, mem_bank_Q2 pipeline */
begin

```

```

    mem_bank_Q <= mem_bank;    // Delay by 1 clock
    mem_bank_Q2 <= mem_bank_Q; // Delay by 2 clocks
end

```

```

always @ (posedge clk, negedge rst)
    if(!rst)
        enable_tbu_0 <= 1'b0;
    else if(mem_bank_Q2==2'b10)
        enable_tbu_0 <= 1'b1;

```

```

always @ (posedge clk, negedge rst)
    if(!rst)
        enable_tbu_1 <= 1'b0;
    else if(mem_bank_Q2==2'b11)
        enable_tbu_1 <= 1'b1;

```

```

always @ (posedge clk)
    case(mem_bank_Q2)
        2'b00:    begin
            d_in_0_tbu_0 <= d_o_mem_D;
            d_in_1_tbu_0 <= d_o_mem_C;

            d_in_0_tbu_1 <= d_o_mem_C;
            d_in_1_tbu_1 <= d_o_mem_B;

            selection_tbu_0<= 1'b0;
            selection_tbu_1<= 1'b1;

```

```

        end
        2'b01:    begin
            d_in_0_tbu_0 <= d_o_mem_D;
            d_in_1_tbu_0 <= d_o_mem_C;

            d_in_0_tbu_1 <= d_o_mem_A;
            d_in_1_tbu_1 <= d_o_mem_D;

            selection_tbu_0<= 1'b1;
            selection_tbu_1<= 1'b0;

```

```

        end
        2'b10:    begin
            d_in_0_tbu_0 <= d_o_mem_B;
            d_in_1_tbu_0 <= d_o_mem_A;

            d_in_0_tbu_1 <= d_o_mem_A;
            d_in_1_tbu_1 <= d_o_mem_D;

            selection_tbu_0<= 1'b0;
            selection_tbu_1<= 1'b1;

```

```

end
2'b11:    begin
    d_in_0_tbu_0  <= d_o_mem_B;
    d_in_1_tbu_0  <= d_o_mem_A;

    d_in_0_tbu_1  <= d_o_mem_C;
    d_in_1_tbu_1  <= d_o_mem_B;

    selection_tbu_0<= 1'b1;
    selection_tbu_1<= 1'b0;
end
endcase

```

//Trace-Back modules instantiation

```

tbu tbu_0 (
    .clk,
    .rst,
    .enable(enable_tbu_0),
    .selection(selection_tbu_0),
    .d_in_0(d_in_0_tbu_0),
    .d_in_1(d_in_1_tbu_0),
    .d_o(d_o_tbu_0),
    .wr_en(wr_disp_mem_0)
);

```

/* analogous for tbu_1
*/

```

tbu tbu_1 (
    .clk(clk),
    .rst(rst),
    .enable(enable_tbu_1),
    .selection(selection_tbu_1),
    .d_in_0(d_in_0_tbu_1),
    .d_in_1(d_in_1_tbu_1),
    .d_o(d_o_tbu_1),
    .wr_en(wr_disp_mem_1)
);

```

//Display Memory modules Instantioation

```

// d_in_disp_mem_K = d_o_tbu_K; K=0,1
assign d_in_disp_mem_0 = d_o_tbu_0;
assign d_in_disp_mem_1 = d_o_tbu_1;

```

```

mem_disp disp_mem_0 (
    .clk(clk),

```

```

        .wr(wr_disp_mem_0),
        .addr(addr_disp_mem_0),
        .d_i(d_in_disp_mem_0),
        .d_o(d_o_disp_mem_0)
    );
/* analogous for disp_mem_1
*/
    mem_disp disp_mem_1 (
        .clk(clk),
        .wr(wr_disp_mem_1),
        .addr(addr_disp_mem_1),
        .d_i(d_in_disp_mem_1),
        .d_o(d_o_disp_mem_1)
    );

// Display memory module operation
always @ (posedge clk)
    mem_bank_Q3 <= mem_bank_Q2[0];

always @ (posedge clk)
    if(!rst)
        wr_mem_counter_disp <= 10'd2; //min value + 2
    else if(!enable)
        wr_mem_counter_disp <= 10'd2; //same
    else
        wr_mem_counter_disp <= wr_mem_counter_disp - 1; // decrement
wr_mem_counter_disp

always @ (posedge clk)
    if(!rst)
        rd_mem_counter_disp <= 10'd1021; //max value - 2
    else if(!enable)
        rd_mem_counter_disp <= 10'd1021; //same
    else
        rd_mem_counter_disp <= rd_mem_counter_disp + 1; // increment
rd_mem_counter_disp

always @ (posedge clk)
    begin
        // if !mem_bank_Q3
        if (!mem_bank_Q3)
            begin
                addr_disp_mem_0 <= rd_mem_counter_disp;
                addr_disp_mem_1 <= wr_mem_counter_disp;
            end
        // else: swap rd and wr
        else begin

```



```

        addr_disp_mem_0 <= wr_mem_counter_disp;
        addr_disp_mem_1 <= rd_mem_counter_disp;
    end
end

    always @ (posedge clk)    begin
/* pipeline mem_bank_Q3 to Q4 to Q5
also d_out = d_o_disp_mem_i
i = mem_bank_Q5 */
        mem_bank_Q4 <= mem_bank_Q3;
        mem_bank_Q5 <= mem_bank_Q4;
        if (mem_bank_Q5)
            d_out <= d_o_disp_mem_1;
        else
            d_out <= d_o_disp_mem_0;
        end
end

```

endmodule

b. bmc0

```

/* For our constraint length = 3, there will be  $2^{*3} = 8$ 
of these, but unlike ACS, not all are identical.
*/

```

```

module bmc0                                // branch metric computation
(
    input  [1:0] rx_pair,
    output [1:0] path_0_bmc,
    output [1:0] path_1_bmc);

//Fill in the guts per BMC instructions
    logic tmp00, tmp01;
    logic tmp10, tmp11;

    assign tmp00 = rx_pair[0];
    assign tmp01 = rx_pair[1];
    assign tmp10 = !tmp00;
    assign tmp11 = !tmp01;

    assign path_0_bmc[1] = tmp00 & tmp01;
    assign path_0_bmc[0] = tmp00 ^ tmp01;
    assign path_1_bmc[1] = tmp10 & tmp11;
    assign path_1_bmc[0] = tmp10 ^ tmp11;

endmodule

```

c. bmc1

```

/* For our constraint length = 3, there will be  $2^{*3} = 8$ 

```

of these, but unlike ACS, not all are identical.

*/

```
module bmc1                                // branch metric computation
```

```
(
```

```
  input  [1:0] rx_pair,
```

```
  output [1:0] path_0_bmc,
```

```
  output [1:0] path_1_bmc);
```

```
//Fill in the guts per BMC instructions
```

```
  logic tmp00, tmp01;
```

```
  logic tmp10, tmp11;
```

```
    assign tmp00 = rx_pair[0];
```

```
    assign tmp01 = !rx_pair[1];
```

```
    assign tmp10 = !tmp00;
```

```
    assign tmp11 = !tmp01;
```

```
    assign path_0_bmc[1] = tmp00 & tmp01;
```

```
    assign path_0_bmc[0] = tmp00 ^ tmp01;
```

```
    assign path_1_bmc[1] = tmp10 & tmp11;
```

```
    assign path_1_bmc[0] = tmp10 ^ tmp11;
```

```
endmodule
```

d. acs

```
module ACS                                // add-compare-select
```

```
( input  path_0_valid,
```

```
  input  path_1_valid,
```

```
  input [1:0] path_0_bmc,
```

```
                                // branch metric computation
```

```
  input [1:0] path_1_bmc,
```

```
  input [7:0] path_0_pmc,
```

```
                                // path metric
```

```
computation(before)
```

```
  input [7:0] path_1_pmc,
```

```
  output logic    selection,
```

```
  output logic    valid_o,
```

```
  output logic [7:0] path_cost);
```

```
  wire [7:0] path_cost_0;
```

```
                                // branch metric + path metric
```

```
  wire [7:0] path_cost_1;
```

```
// Fill in the guts per ACS instructions
```

```
  assign path_cost_0 = path_0_pmc + path_0_bmc;
```

```
  assign path_cost_1 = path_1_pmc + path_1_bmc;
```

```
/* always_comb begin
```

```
  case ({path_1_valid, path_0_valid})
```

```

2'b00: begin
    // both path are invalid
    valid_o = 1'b0;
    selection = 1'b0;
    path_cost = 8'd0;
end
2'b01: begin
    // path1 is valid
    valid_o = 1'b1;
    selection = 1'b0;
    path_cost = path_cost_0;
end
2'b10: begin
    // path 0 is valid
    valid_o = 1'b1;
    selection = 1'b1;
    path_cost = path_cost_1;
end
2'b11: begin
    // both are valid
    valid_o = 1'b1;
    if (path_cost_0 > path_cost_1) begin
        selection = 1'b1;
        path_cost = path_cost_1;
    end else begin
        selection = 1'b0;
        path_cost = path_cost_0;
    end
end
default: begin
    valid_o = 1'b0;
    selection = 1'b0;
    path_cost = 8'd0;
end
endcase
end

*/
assign path_cost = (valid_o?(selection?path_cost_1:path_cost_0):8'd0);
assign valid_o=path_0_valid | path_1_valid;

/* always_comb begin
    if(valid_o==0) path_cost=8'b0;
    else if(valid_o==1 && selection==0)path_cost=path_cost_0;
    else if(valid_o==1 && selection==1)path_cost=path_cost_1;
end

*/
always_comb begin
    if (path_0_valid == 1'b0 && path_1_valid == 1'b1) selection = 1'b1;

```

```

else if (path_0_valid == 1'b1 && path_1_valid == 1'b0) selection =
1'b0;

else if (path_0_valid == 1'b1 && path_1_valid == 1'b1) begin
if (path_cost_0 > path_cost_1) selection = 1'b1;
else selection = 1'b0;
end
else selection=1'b0;
end
end

```

```
endmodule
```

e. mem_1x1024

```

/*make the data path K bits wide for mem_Kx1024
K=8 for module mem, K=1 for module mem_disp */
module mem_disp (
input      clk,
input      wr, // write enable
input  [9:0]  addr, // 2^10=1024
input      d_i,      // data
output logic d_o);

logic      mem [0:1023];

always @ (posedge clk) begin
/*
write synchronously to memory core if enabled
read synchronously at all times (equiv. to DFF at mem data out)
*/
if(wr)begin
mem[addr] <= d_i;
end
d_o <= mem[addr];
end
endmodule

```

f. mem_8x1024

```

module mem (
input      clk,
input      wr, // write enable
input  [9:0]  addr, // 2^10=1024
input  [7:0]  d_i, // data input (8-bit)
output logic [7:0] d_o // data output (8-bit)
);

logic [7:0] mem [0:1023]; // 1024 x 8-bit memory array

always @ (posedge clk) begin
// Write synchronously to memory core if enabled
// Read synchronously at all times (equiv. to DFF at mem data out)

```

```

        if(wr) begin
            mem[addr] <= d_i;
        end
        d_o <= mem[addr];
    end
endmodule

g. tbu
module tbu (
    input        clk,
    input        rst,
    input        enable,
    input        selection,
    input  [7:0]  d_in_0,
    input  [7:0]  d_in_1,
    output logic  d_o,
    output logic  wr_en
);

    logic  d_o_reg;
    logic  wr_en_reg;

    logic [2:0] pstate;
    logic [2:0] nstate;

    logic  selection_buf;

    always @(posedge clk) begin
        selection_buf <= selection;
        wr_en         <= wr_en_reg;
        d_o           <= d_o_reg;
    end
    ///reset p state to 0
    //exception: rst = enable = selection_buf = 1, but selection = 0, then go to n_state
    always @(posedge clk, negedge rst) begin
        if (!rst) begin
            pstate <= 3'd0;
        end else if (enable && selection_buf && !selection) begin
            pstate <= nstate;
        end else if (enable) begin
            pstate <= nstate;
        end
    end

    always_comb begin
        wr_en_reg = selection;
        //d_o_reg = selection ? d_in_1[pstate] : d_in_0[pstate];
        if(selection)d_o_reg=d_in_1[pstate];
        //else if(!selection) d_o_reg=d_in_0[pstate];
    end

```

else d_o_reg=0;

```
case (pstate)
  3'd0: begin
    if (selection_buf) begin
      if (d_in_1[pstate] == 1'b0) nstate = 3'd0; else nstate = 3'd1;
    end else begin
      if (d_in_0[pstate] == 1'b0) nstate = 3'd0; else nstate = 3'd1;
    end
  end
  3'd1: begin
    if (selection_buf) begin
      if (d_in_1[pstate] == 1'b0) nstate = 3'd3; else nstate = 3'd2;
    end else begin
      if (d_in_0[pstate] == 1'b0) nstate = 3'd3; else nstate = 3'd2;
    end
  end
  3'd2: begin
    if (selection_buf) begin
      if (d_in_1[pstate] == 1'b0) nstate = 3'd4; else nstate = 3'd5;
    end else begin
      if (d_in_0[pstate] == 1'b0) nstate = 3'd4; else nstate = 3'd5;
    end
  end
  3'd3: begin
    if (selection_buf) begin
      if (d_in_1[pstate] == 1'b0) nstate = 3'd7; else nstate = 3'd6;
    end else begin
      if (d_in_0[pstate] == 1'b0) nstate = 3'd7; else nstate = 3'd6;
    end
  end
  3'd4: begin
    if (selection_buf) begin
      if (d_in_1[pstate] == 1'b0) nstate = 3'd1; else nstate = 3'd0;
    end else begin
      if (d_in_0[pstate] == 1'b0) nstate = 3'd1; else nstate = 3'd0;
    end
  end
  3'd5: begin
    if (selection_buf) begin
      if (d_in_1[pstate] == 1'b0) nstate = 3'd2; else nstate = 3'd3;
    end else begin
      if (d_in_0[pstate] == 1'b0) nstate = 3'd2; else nstate = 3'd3;
    end
  end
  3'd6: begin
    if (selection_buf) begin
      if (d_in_1[pstate] == 1'b0) nstate = 3'd5; else nstate = 3'd4;
```

```

        end else begin
            if (d_in_0[pstate] == 1'b0) nstate = 3'd5; else nstate = 3'd4;
        end
    end
3'd7: begin
    if (selection_buf) begin
        if (d_in_1[pstate] == 1'b0) nstate = 3'd6; else nstate = 3'd7;
    end else begin
        if (d_in_0[pstate] == 1'b0) nstate = 3'd6; else nstate = 3'd7;
    end
    end
default: begin
    nstate = 3'd0;
end
endcase
end

endmodule

```